

# VLSI

October 20<sup>th</sup> 2023

**Due date: November 3<sup>rd</sup> 2023**

Name: \_\_\_\_\_ DU ID: \_\_\_\_\_ Section: \_\_\_\_\_

## Lab 5 – Directions

### Part 1

Draft schematics, layouts, and symbols for a 2-input NAND gate and a 2-input XOR gate using 6u/2u MOSFETs (both NMOS and PMOS)

- Ensure that your symbol views are commonly used symbols (not boxes) for these gates with your initials in the middle of the symbol
- Ensure all layouts in this lab use standard cell frames that snap together end-to-end for routing vdd and gnd.
- Ensure gate inputs, outputs, vdd, and gnd are all routed in metal1
- Simulate the logic operation of the gates for all 4 possible inputs (00, 01, 10, 11).
- Comment on how timing of the input pulses can cause glitches in the output of a gate.
- DRC and NCC your designs

### Part 2

Using the gates from Part 1, draft the schematic, layout, and symbol of a full adder (truth table and circuit below).

- Simulate the operation of the full adder
- Layout the full adder by placing the 5 gates end-to-end so that vdd and gnd are routed
- Full adder inputs and outputs can be on metal 2 but not metal 3
- DRC and NCC your designs

Your lab report should document the all process of building and simulating the circuits from Part 1 and Part2.

Don't forget to include all necessary explanations to support all the decisions taken during the design of the schematics, layouts and simulations.

**Good luck and have fun.**

### Auxiliary Pictures

a	b	cin	cout	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Figure 1 - Full Adder Truth Table

 


Figure 2 - Full Adder Circuit